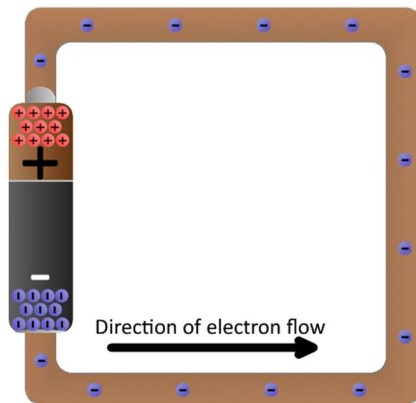


ARDUINO

1. ELEKTER

- a. **OVERALL PRACTICAL** <https://learn.sparkfun.com/tutorials/what-is-electricity> - Üldine, hea ja tutvustav
 - i. ATOM
 - 1. ELECTRON –
 - 2. PROTONS +
 - 3. NEUTRONS 0
 - ii. Potential/Kinetic
 - iii. Current
 - iv. FIELDS
 - v. Voltage – The difference of potential energy between points in a electrical field.
 - vi. Resistance
 - 1. Conductors
 - 2. Insulators
 - vii. FIELDS
- b. **OVERALL PRACTICAL** https://www.newark.com/wcsstore/ExtendedSitesCatalogAssetStore/cms/asset/images/americas/common/storefront/eaton_cutler_hammer/101-Elec-Basics.pdf
 - i. Current – The number of electron that flow through a cross section in one second. (Measured in Amperes.) (Notation I)
 - ii. Voltage – The force, that is applied to conductor to free electrons. This causes the electrical current to flow. (Measured in Volts.) (Notation E)
 - iii. Resistance – Based on length, material, temperature, width (Notation R)
 - iv. Ohms Law – $E=IR$
- c. **OVERALL THEORETICAL** <https://www.khanacademy.org/science/physics/electric-charge-electric-force-and-voltage> Again a very high level tutorial from KHAN academy for theory of electricity. Also with some mathematics. Calculus, e.g integrals used.
- d. **GROUND** Ground in this Picture is the plus side, because it has the lowest potential energy. In terms of pushing from - side. Also there the electrons will be neutralized by the protons. In the case, we have no resistance inbetween the conductor and the source, bad things will happen..




After a second of the current flow, the electrons have actually moved *very* little—fractions of a centimeter. However, the energy produced by the current flow is *huge*, especially since there's nothing in this circuit to slow down the flow or consume the energy. Connecting a pure conductor directly across an energy source is a **bad idea**. Energy moves very quickly through the system and is transformed into heat in the wire, which may quickly turn into melting wire or fire.

- e. **OVERALL THEORETICAL, PRACTICAL** <http://www.allaboutcircuits.com/textbook/direct-current/chpt-1/voltage-current/>

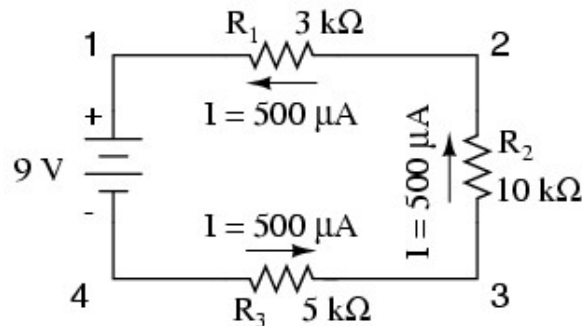- i. **SINGLE CIRCUITS** <http://www.allaboutcircuits.com/textbook/direct-current/chpt-5/simple-series-circuits/>

In the beginning we only have total voltage and resistance and also the resistances of each separate resistance. We add R_1 , R_2 , R_3 up to get total resistance. Then based on total voltage and total resistance we calculate amps $I = E/R$. As I is the same everywhere, we can calculate the separate voltages based on I and separate Resistances. This adds up to nine.




	R_1	R_2	R_3	Total	
E	1.5	5	2.5	9	Volts
I	500μ	500μ	500μ	500μ	Amps
R	3k	10k	5k	18k	Ohms

↑
Ohm's Law

↑
Ohm's Law

↑
Ohm's Law

ii. PARALLEL CIRCUITS

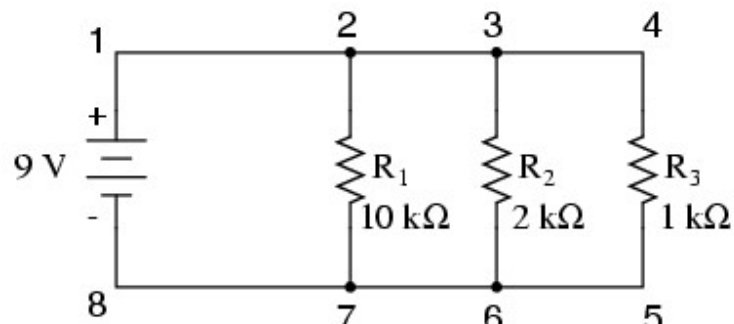

	R ₁	R ₂	R ₃	Total	
E	9	9	9	9	Volts
I	0.9m	4.5m	9m	14.4m	Amps
R	10k	2k	1k	625	Ohms

$$R_{\text{total}} = \frac{E_{\text{total}}}{I_{\text{total}}} = \frac{9 \text{ V}}{14.4 \text{ mA}} = 625 \Omega$$

\uparrow
Ohm's Law

[PROJECT 1 IN ARDUINO PROJECT BOOK.](#)

[PROJECT 2 IN ARDUINO PROJECT BOOK.](#)

[PROJECT 3 IN ARDUINO PROJECT BOOK.](#)

[PROJECT 4 IN ARDUINO PROJECT BOOK.](#)